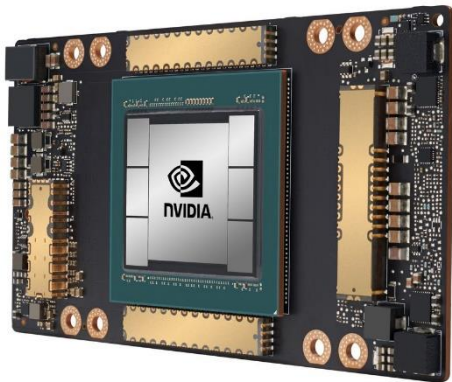



CSCB58: Computer Organization



Prof. Gennady Pekhimenko

University of Toronto

Fall 2020

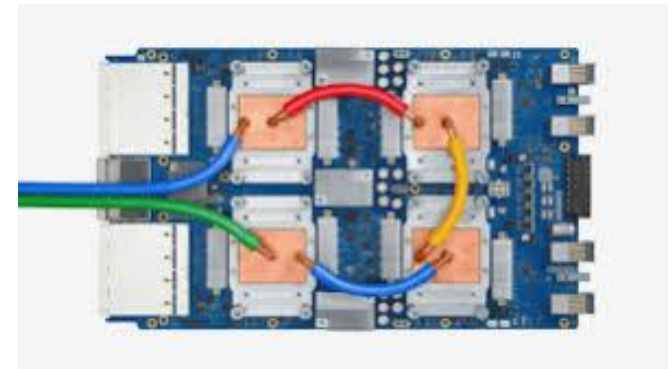

*The content of this lecture is adapted from the lectures of
Larry Zheng and Steve Engels*

CSCB58 Week 3: Summary

Week 3 review

- Building
 - Mux/demux
 - Decoders
 - Adders
 - Subtractors
 - Comparators

Comparators



Comparators

- A circuit that takes in two input vectors, and determines if the first is greater than, less than or equal to the second.
- How does one make that in a circuit?



Basic Comparators

- Consider two binary numbers A and B, where A and B are one bit long.
- The circuits for this would be:

- $A=B$:


$$A \cdot B + \bar{A} \cdot \bar{B}$$

- $A>B$:

$$A \cdot \bar{B}$$

- $A<B$:


$$\bar{A} \cdot B$$

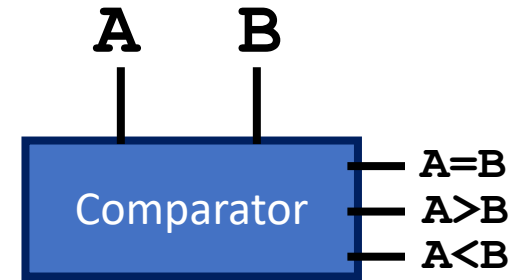

A	B
0	0
0	1
1	0
1	1

Basic Comparators

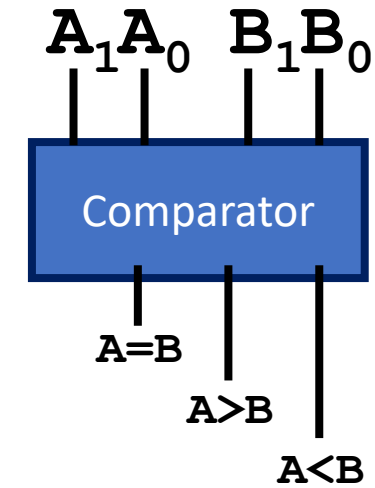- What if A and B are two bits long?
- The terms for this circuit for have to expand to reflect the second signal.
- For example:



- $A==B$:


$$(A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_0 \cdot B_0 + \bar{A}_0 \cdot \bar{B}_0)$$

Make sure that the values
of bit 1 are the same

Make sure that the values
of bit 0 are the same

Basic Comparators

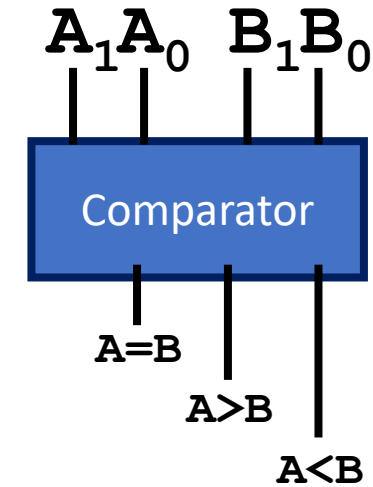- What about checking if A is greater than B?



- $A > B$:

$$A_1 \cdot \bar{B}_1 + (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_0 \cdot \bar{B}_0)$$


Check if first bit satisfies condition



If not, check that the first bits are equal...



...and then do the 1-bit comparison

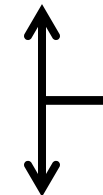

- $A < B$:

$$\bar{A}_1 \cdot B_1 + (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (\bar{A}_0 \cdot B_0)$$

$A > B$ if and only if $A_1 > B_1$ or $(A_1 = B_1$ and $A_0 > B_0)$

General Comparators

- The general circuit for comparators requires you to define equations for each case.

- Case #1: Equality

- If inputs A and B are equal, then all bits must be the same.

- Define X_i for any digit i :

- (equality for digit i)

$$X_i = A_i \cdot B_i + \bar{A}_i \cdot \bar{B}_i$$

- Equality between A and B is defined as:

$$A==B : X_0 \cdot X_1 \cdot \dots \cdot X_n$$

Comparators

- Case #2: $A > B$
 - The first non-matching bits occur at bit i , where $A_i=1$ and $B_i=0$. All higher bits match.
 - Using the definition for X_i from before:

$$A > B = A_n \cdot \bar{B}_n + X_n \cdot A_{n-1} \cdot \bar{B}_{n-1} + \dots + A_0 \cdot \bar{B}_0 \cdot \prod_{k=1}^n X_k$$

- Case #3: $A < B$
 - The first non-matching bits occur at bit i , where $A_i=0$ and $B_i=1$. Again, all higher bits match.

$$A < B = \bar{A}_n \cdot B_n + X_n \cdot \bar{A}_{n-1} \cdot B_{n-1} + \dots + \bar{A}_0 \cdot B_0 \cdot \prod_{k=1}^n X_k$$

Comparator truth table

- Given two input vectors of size $n=2$, output of circuit is shown at right.

Inputs				Outputs		
A_1	A_0	B_1	B_0	$A < B$	$A = B$	$A > B$
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

Comparator example (cont'd)

$A < B$:

	$\bar{B}_0 \cdot \bar{B}_1$	$B_0 \cdot \bar{B}_1$	$B_0 \cdot B_1$	$\bar{B}_0 \cdot B_1$
$\bar{A}_0 \cdot \bar{A}_1$	0	1	1	1
$A_0 \cdot \bar{A}_1$	0	0	1	1
$A_0 \cdot A_1$	0	0	0	0
$\bar{A}_0 \cdot A_1$	0	0	1	0

$$LT = B_1 \cdot \bar{A}_1 + B_0 \cdot B_1 \cdot \bar{A}_0 + B_0 \cdot \bar{A}_0 \cdot \bar{A}_1$$

Comparator example (cont'd)

$A=B$:

	$\bar{B}_0 \cdot \bar{B}_1$	$B_0 \cdot \bar{B}_1$	$B_0 \cdot B_1$	$\bar{B}_0 \cdot B_1$
$\bar{A}_0 \cdot \bar{A}_1$	1	0	0	0
$A_0 \cdot \bar{A}_1$	0	1	0	0
$A_0 \cdot A_1$	0	0	1	0
$\bar{A}_0 \cdot A_1$	0	0	0	1

$$EQ = \bar{B}_0 \cdot \bar{B}_1 \cdot \bar{A}_0 \cdot \bar{A}_1 + B_0 \cdot \bar{B}_1 \cdot A_0 \cdot \bar{A}_1 + B_0 \cdot B_1 \cdot A_0 \cdot A_1 + \bar{B}_0 \cdot B_1 \cdot \bar{A}_0 \cdot A_1$$

Comparator example (cont'd)


$A > B$:

	$\bar{B}_0 \cdot \bar{B}_1$	$B_0 \cdot \bar{B}_1$	$B_0 \cdot B_1$	$\bar{B}_0 \cdot B_1$
$\bar{A}_0 \cdot \bar{A}_1$	0	0	0	0
$A_0 \cdot \bar{A}_1$	1	0	0	0
$A_0 \cdot A_1$	1	1	0	1
$\bar{A}_0 \cdot A_1$	1	1	0	0

$$GT = \bar{B}_1 \cdot A_1 + \bar{B}_0 \cdot \bar{B}_1 \cdot A_0 + \bar{B}_0 \cdot A_0 \cdot A_1$$

Comparing larger numbers

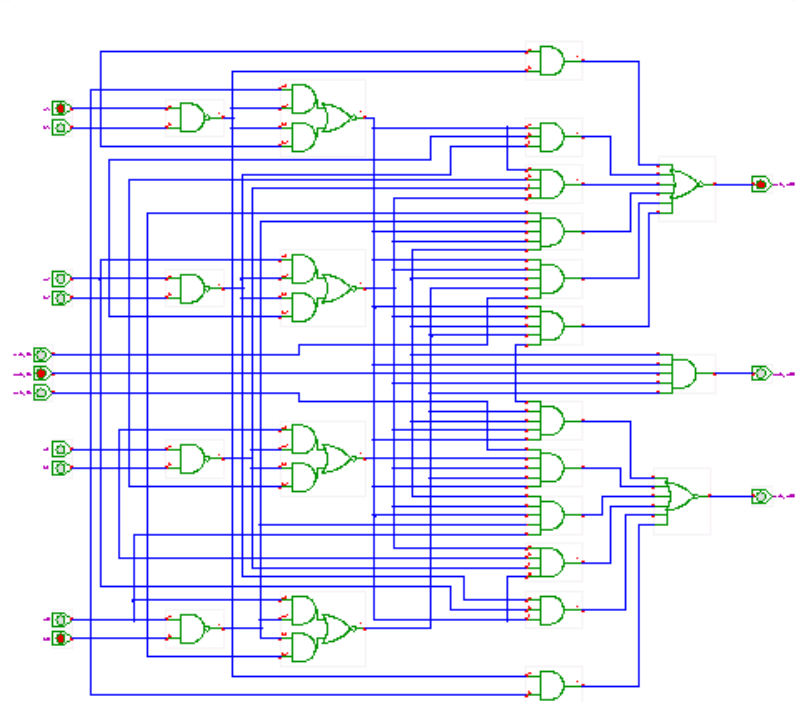- As numbers get larger, the comparator circuit gets more complex.
- At a certain level, it can be easier sometimes to just process the result of a subtraction operation instead.
 - Easier, less circuitry, just not faster.



Question #1

- a) How do you write the number 78 as an 8-bit binary number?

128	64	32	16	8	4	2	1
0	1	0	0	1	1	1	0

- b) What is the two's complement of 01101101?

10010011

- c) What is the sum of 01101101 and 01101101?

11011010

← Note what's happening here!

Question #2


- What groupings are in the K-map on the right?

	$\bar{C} \cdot \bar{D}$	$C \cdot \bar{D}$	$C \cdot D$	$\bar{C} \cdot D$
$\bar{A} \cdot \bar{B}$	1	1	X	1
$A \cdot \bar{B}$	X	0	X	1
$A \cdot B$	1	X	X	1
$\bar{A} \cdot B$	1	X	0	X

- What logic equations do these groupings represent?

$$\bar{A} \cdot \bar{B} + \bar{C}$$


CSCB58: Computer Organization

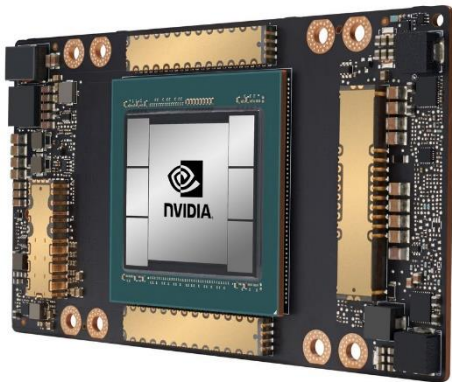

Prof. Gennady Pekhimenko

University of Toronto

Fall 2020

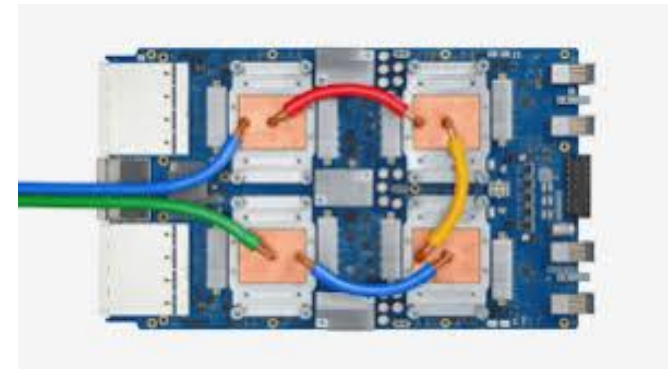

*The content of this lecture is adapted from the lectures of
Larry Zheng and Steve Engels*